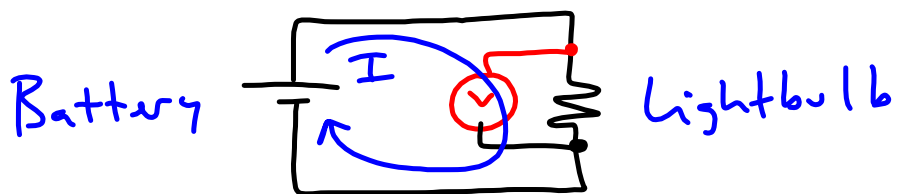


MORE CIRCUITS

- Materials
 - 2 boards
 - 1 battery/holder
 - 3 light bulb/holders
 - wires (red and black)
 - multimeter with plug-to-clips


- Simple Series Circuit




Multimeter (orange device) → 2V
- Red lead in V·Ω·mA·Temp plug
- Black in COM

- Electric Potential Energy
 - Energy stored electrically with the ability to move e^-
 - Hard to measure directly
- Electric Potential
 - Much easier to measure, based on definition
 - Known as "voltage"
- ★ - Measure ACROSS pieces

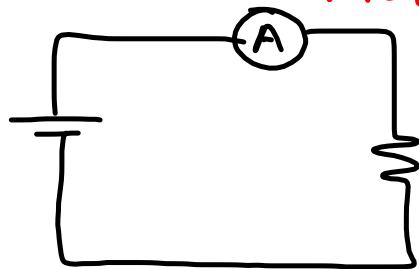- Measuring Current
 - Setting \rightarrow 200mA



multimeter

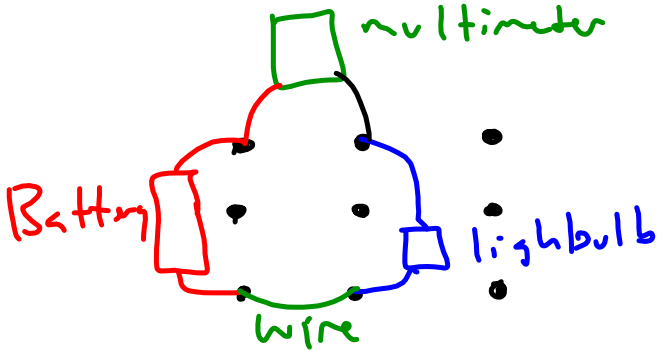

BEFORE CHANGING SETTINGS,
UNCLIP LEADS

- Ohm's Law

- $V = IR$

- Electric potential = (current)(resistance)

- What is the resistance of your lightbulb?

calculated


$$R = \frac{V}{I} = \frac{1.3V}{0.06A} = 21.7 \Omega$$

measure R

- Public Safety Announcement

$$I = \frac{V}{R}$$

- Next circuit

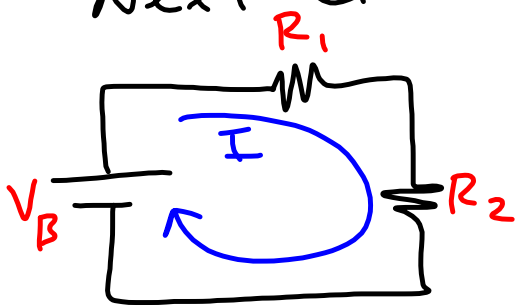

| | <u>Measure</u> | <u>Calculate</u> |
|-------|-----------------|------------------|
| I | 0.055A | |
| V_1 | 0.67V | |
| V_2 | 0.63V | |
| V_B | 1.3V | |

$$V_B = V_1 + V_2$$

- Equivalent Resistance:

- Way to combine resistors to calculate parts of a circuit


- Series $\rightarrow R_{eq} = R_1 + R_2 + \dots$

- Parallel $\rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

$R_{eq} < \text{lowest-valued resistor}$

$$\frac{1}{R_{eq}} = \frac{1}{10\Omega} + \frac{1}{5\Omega} \Rightarrow R_{eq} = 3.33\Omega$$

• Next circuit

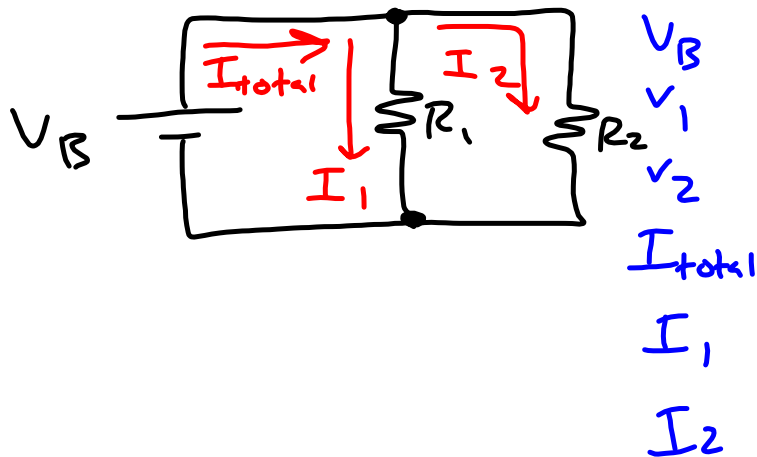

Measure

Calculate

$$V_B = V_1 = V_2$$

$$I_{total} = I_1 + I_2$$