

REVIEW - ELECTROSTATICS AND CIRCUITS

- Charge of proton/electron $\rightarrow \pm 1.6 \times 10^{-19} \text{ C}$
- Like charges repel; unlike charges attract

- Equations

- Coulomb's Law: $F = \frac{kq_1q_2}{r^2}$

$$k = 9 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2}$$

direction comes from drawing

- Current: $I = \frac{\Delta q}{\Delta t}$

$$1 \text{ Ampere} \equiv 1 \frac{\text{coulomb}}{\text{second}}$$

- Ohm's Law: $V = IR$

- Electric Power: $P = IV = I^2R = \frac{V^2}{R}$


- Equivalent Resistance

- Series: $R_{eq} = R_1 + R_2 + \dots$

- Parallel: $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

- Variables: [Units]
 - $F \rightarrow$ Force [Newtons $\rightarrow N$]
 - $q \rightarrow$ charge [Coulombs $\rightarrow C$]
 - $r \rightarrow$ distance between charged particles [meters $\rightarrow m$]
 - $t \rightarrow$ time [seconds $\rightarrow s$]
 - $I \rightarrow$ current [Amperes $\rightarrow A$]
 - $V \rightarrow$ electric potential (voltage, voltage drop) [Volts $\rightarrow V$]
 - $R \rightarrow$ resistance [Ohms $\rightarrow \Omega$]
 - $P \rightarrow$ power [Watts $\rightarrow W$]
 - $R_{eq} \rightarrow$ equivalent resistance [ohms $\rightarrow \Omega$]

Review Sheet

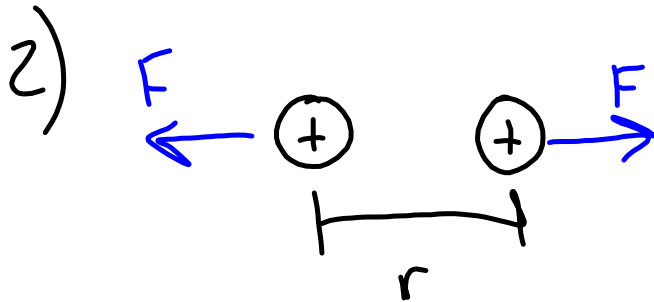

$$F = \frac{kq_1q_2}{r^2}$$

$$F = 105 \text{ N}$$

$$k = 9 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2}$$

$$q_1 = 4 \times 10^{-6} \text{ C}$$

$$q_2 = 4 \times 10^{-6} \text{ C}$$


$$r = \sqrt{\frac{kq_1q_2}{F}}$$

$$= \sqrt{\frac{(9 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2})(4 \times 10^{-6} \text{ C})(4 \times 10^{-6} \text{ C})}{105 \text{ N}}}$$

$$= 0.037 \text{ m}$$

Power And Parallel Circuits

7) a.

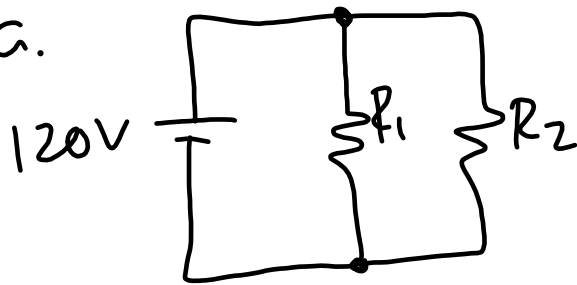
 $R_1 \rightarrow$ blender
(400W)

 $R_2 \rightarrow$ coffee maker

$$b) \quad P_1 = I_1 V$$

$$I_1 = \frac{P_1}{V}$$

$$= \frac{400 \text{ W}}{120 \text{ V}}$$

$$= 3.33 \text{ A}$$

$$P_2 = I_2 V$$

$$I_2 = \frac{P_2}{V}$$

$$= \frac{900 \text{ W}}{120 \text{ V}}$$

$$= 7.5 \text{ A}$$

$$I_{\text{total}} = I_1 + I_2$$

$$= 3.33 \text{ A} + 7.5 \text{ A}$$


$$= 10.83 \text{ A} \quad \text{BREAKER STILL ON!}$$

$$c) \quad I_{\text{Breaker}} = 15 \text{ A}$$

$$I_{\text{extra device}} = 15 \text{ A} - 10.83 \text{ A} = 4.17 \text{ A}$$


$$P_{\text{extradvice}} = V I_{\text{extradvice}} = 500 \text{ W}$$

Combination Circuit

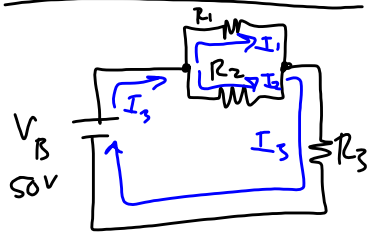


$R_1 = 10\Omega$
 $R_2 = 30\Omega$
 $R_3 = 20\Omega$

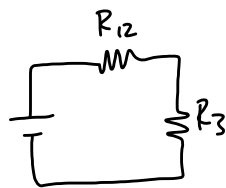Find I_1, I_2, I_3
 V_1, V_2, V_3
 P_1, P_2, P_3




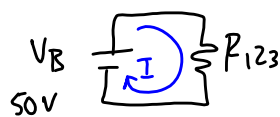$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$
 $R_{12} = 7.5\Omega$




$R_{123} = R_{12} + R_3$
 $= 27.5\Omega$

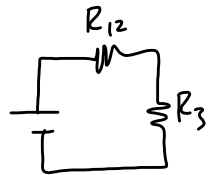$I = \frac{V_B}{R_{123}} = \frac{50V}{27.5\Omega} = 1.82 A$



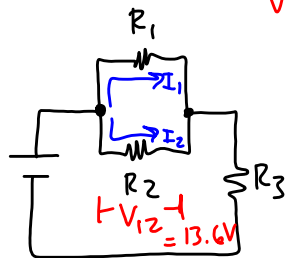$I_3 = 1.82 A$
 $I_{12} = 1.82 A$
 $V_3 = I_3 R_3 = 36.4 V$
 $V_{12} = V_B - V_3 = 13.6 V$




$P_3 = I_3 V_3 = 66.2 W$
 $I_1 = \frac{V_{12}}{R_1} = \frac{13.6V}{10\Omega} = 1.36 A$

$I_2 = \frac{V_{12}}{R_2} = \frac{13.6V}{30\Omega} = 0.45 A$

$I_2 = I_3 - I_1$


$P_1 = I_1 V_1 = 18.5 W$

$P_2 = I_2 V_2 = 6.2 W$

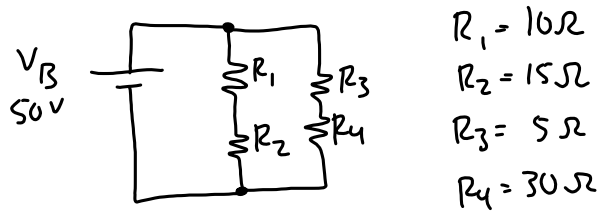


$R_1 = 10\Omega$
 $R_2 = 15\Omega$
 $R_3 = 5\Omega$
 $R_4 = 30\Omega$

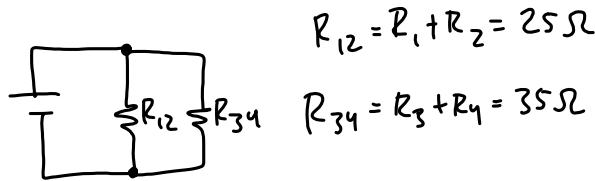Find I_1, I_2, I_3, I_4
 V_1, V_2, V_3, V_4
 P_1, P_2, P_3, P_4



$R_{12} = R_1 + R_2 = 25\Omega$


$R_{34} = R_3 + R_4 = 35\Omega$

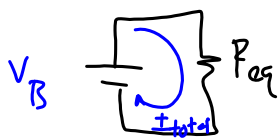

$\frac{1}{R_{eq}} = \frac{1}{R_{12}} + \frac{1}{R_{34}}$

$R_{eq} = 14.58\Omega$

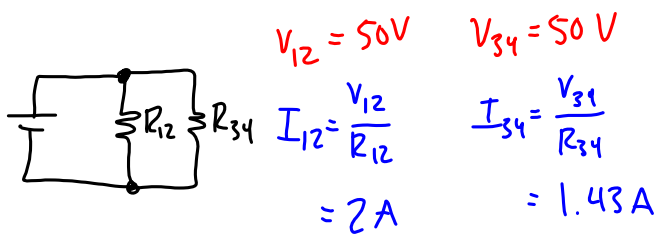$I_{total} = \frac{V_B}{R_{eq}} = 3.43\text{ A}$




$V_{12} = 50\text{ V}$

$V_{34} = 50\text{ V}$

$I_{12} = \frac{V_{12}}{R_{12}}$
 $= 2\text{ A}$

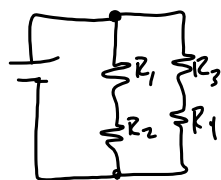$I_{34} = \frac{V_{34}}{R_{34}}$
 $= 1.43\text{ A}$



$I_1 = I_2 = I_{12} = 2\text{ A}$

$I_3 = I_4 = I_{34} = 1.43\text{ A}$

$V_1 = I_{12} R_1 = 20\text{ V}$

$V_3 = I_{34} R_3 = 7.15\text{ V}$

$V_2 = I_{12} R_2 = 30\text{ V}$

$V_4 = I_{34} R_4 = 42.85\text{ V}$

$P_1 = I_{12} V_1 = 40\text{ W}$

$P_3 = I_{34} V_3 = 9.6\text{ W}$

$P_2 = I_{12} V_2 = 60\text{ W}$

$P_4 = I_{34} V_4 = 61.4\text{ W}$

TEST

- Conceptual
 - electric force
 - connecting ammeters and voltmeters
 - Circuits
- Problems
 - Coulomb's Law
 - Series-Only circuit
 - Parallel-Only circuit
 - Combination circuit (four resistors)

