

MORE CIRCUITS

- Materials

- 2 boards


- 1 battery / battery holder

- 3 light bulbs / holders

- Wires

- Multimeter with plug-to-clips


- Simple Series Circuit

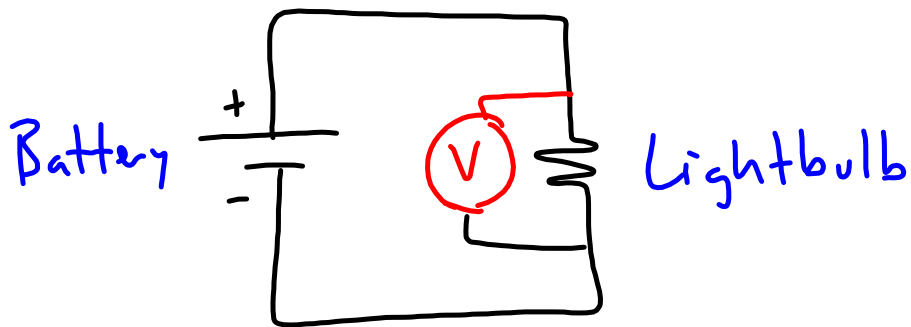

Multimeter → $\overline{\overline{2V}}$

- Red lead in V- Ω -mA-Temp plug
- Black lead in COM

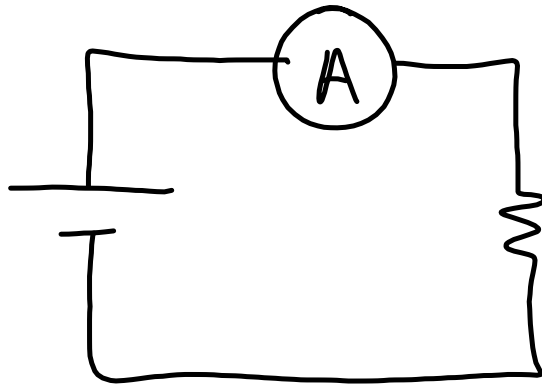- Measuring Current
— Setting \rightarrow 200 mA



- Electric potential energy
 - Energy stored electrically with the ability to move e^-
 - Hard to measure directly
- Electric potential
 - Much easier to measure, based on definition
 - Known as "voltage"
- ★ – Measure across pieces

- Ohm's Law

- $V = IR$

- Electric Potential = (current)
(resistance)

- What is the resistance of your lightbulb?

$$R = \frac{V}{I}$$


$$= \frac{1.247 \text{ V}}{0.06 \text{ A}}$$

$$= 20.8 \Omega$$

- Public Safety Announcement

$$I = \frac{V}{R}$$

• New circuit

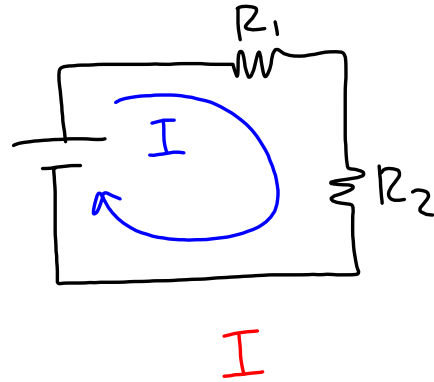

Measure and
Calculate

R_1

R_2

V_1

V_2

$$V_{\text{total}} = V_1 + V_2$$

• Equivalent Resistance

- Way to combine resistors to calculate parts of the circuit

- Series $\rightarrow R_{\text{eq}} = R_1 + R_2 + \dots$


- Parallel $\rightarrow \frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

$R_{\text{eq}} < \text{Lowest-valued resistor}$

$$\text{Ex: } \frac{1}{R_{\text{eq}}} = \frac{1}{10\Omega} + \frac{1}{5\Omega}$$

$$R_{\text{eq}} = 3.33\Omega$$

- Next circuit

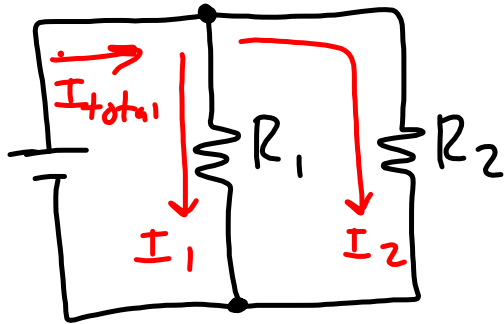

Measure

Calculate

V_{total}

V_1

V_2

I_{total}

I_1

I_2

- All electric potentials are the SAME!

-
$$I_{total} = I_1 + I_2$$