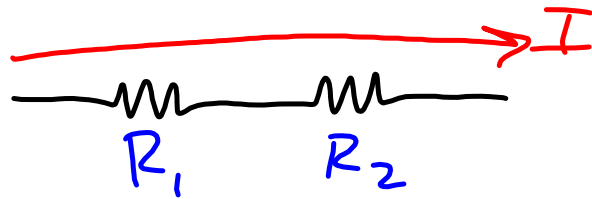


# CIRCUITS


- Equivalent resistance

- Series




$$R_{eq} = R_1 + R_2$$

- Parallel

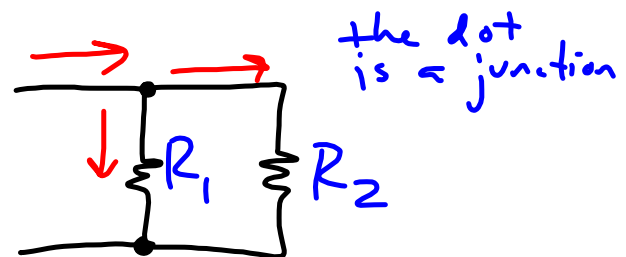

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$R_{eq}$  → equivalent resistance

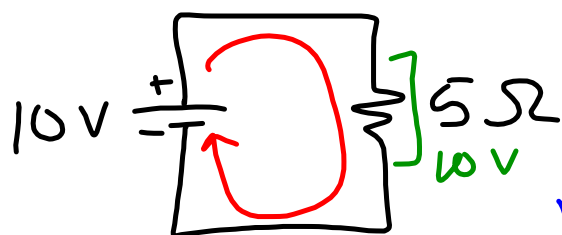


conventional current  
goes from + to -.

$$V = IR$$

$$I = \frac{V}{R} = \frac{10V}{5\Omega} = 2A$$

$V$  across resistor =  $10V$   
(voltage drop)

<u>Variable</u>	<u>Letter</u>	<u>Unit</u>
Electric potential (voltage)	V	Volts (V)
Current	I	Amperes (A)
Resistance	R	Ohms ( $\Omega$ )

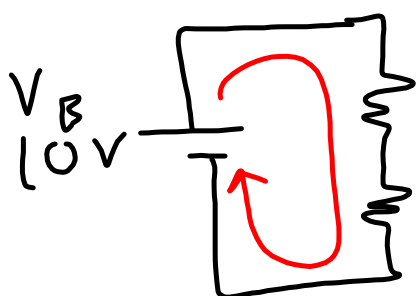

$$R_1 = 7\Omega$$


$$R_2 = 3\Omega$$

$$V_1 = IR_1 = (1A)(7\Omega) = 7V$$

$$V_2 = IR_2 = (1A)(3\Omega) = 3V$$

$$R_{eq} = R_1 + R_2 = 7\Omega + 3\Omega = 10\Omega$$

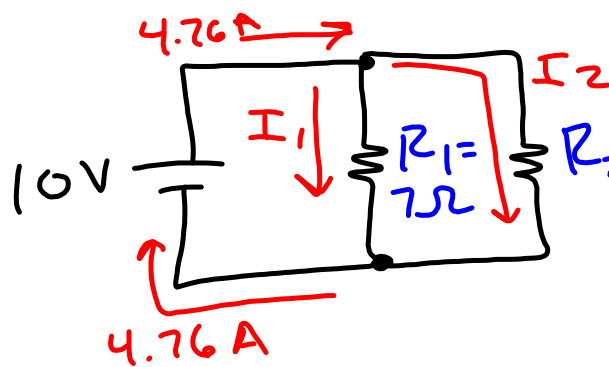
$$I_{total} = \frac{V_B}{R_{eq}} = \frac{10V}{10\Omega} = 1A$$



$$I_{total} = I_1 + I_2$$

$$I_1 = \frac{V_B}{R_1} = \frac{10V}{7\Omega} = 1.4A$$
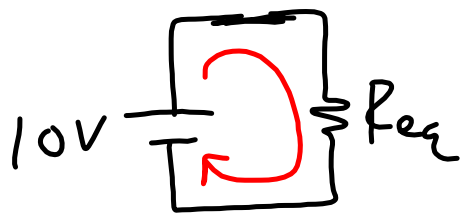
$$I_2 = \frac{V_B}{R_2} = \frac{10V}{3\Omega} = 3.33A$$




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \left[ \frac{1}{7\Omega} + \frac{1}{3\Omega} \right]^{-1}$$

$$= 2.1\Omega$$

$$I_{total} = \frac{V_B}{R_{eq}} = \frac{10V}{2.1\Omega} = 4.76A$$
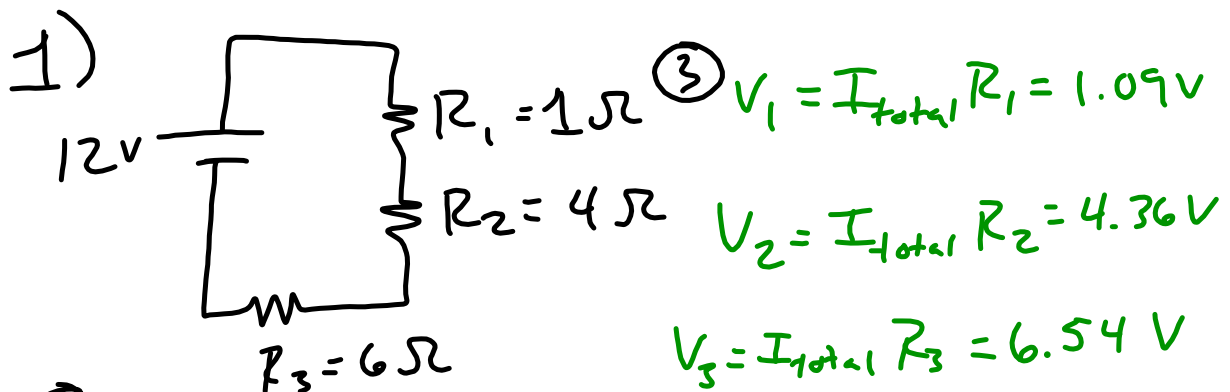
## Practice - Series and Parallel Circuits



①  $R_{eq} = R_1 + R_2 + R_3 = 1\Omega + 4\Omega + 6\Omega = 11\Omega$

②  $I_{total} = \frac{V_B}{R_{eq}} = \frac{12V}{11\Omega} = 1.09A$

