



$$+V_1 - I_1 R_1 - \frac{Q}{C} = 0$$

$$+V_2 - \left(-\frac{Q}{C}\right) - I_2 R = 0$$

$$I_1 = I_2 + I$$

Internal Resistance

