
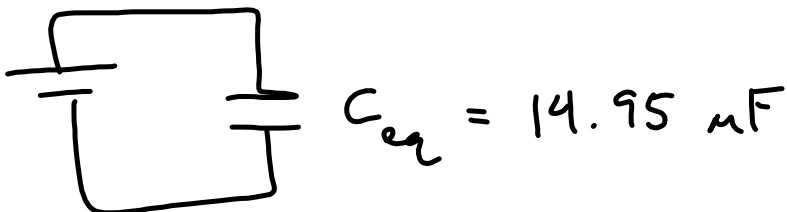
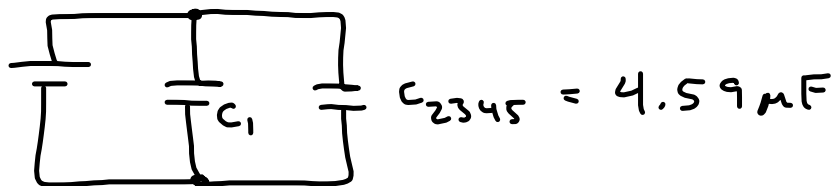
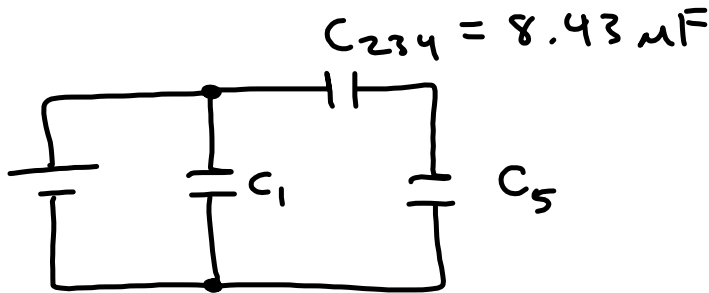
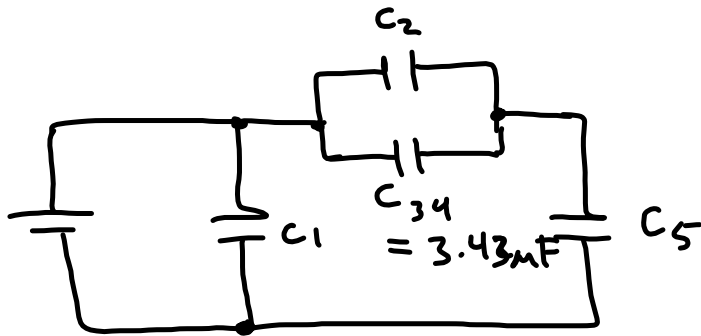


Equivalent Capacitance

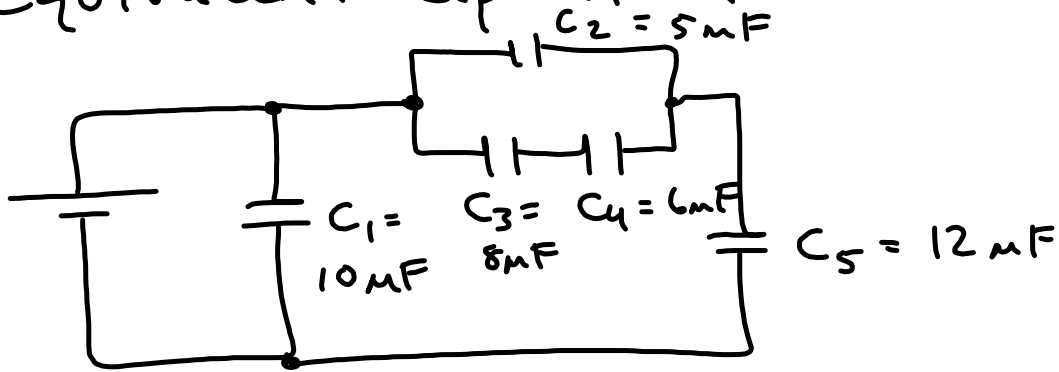

Use $8.85\text{E-}12$ F/m for ϵ_0 . A rectangular capacitor has a capacitance of 0.5 F, dielectric constant of 15 , and separation distance between the plates of 2 mm. If one side of each plate is 1.5 mm, what is the length of the other side?


$$C = \frac{k \epsilon_0 A}{d} \quad A = lw$$

$$C = \frac{k \epsilon_0 lw}{d}$$

$$l = \frac{C d}{k \epsilon_0 w}$$

$$= \frac{(0.5 \cancel{\text{F}})(0.002 \text{ m})}{(15)(8.85\text{E-}12 \cancel{\text{F/m}})(0.0015 \cancel{\text{m}})}$$
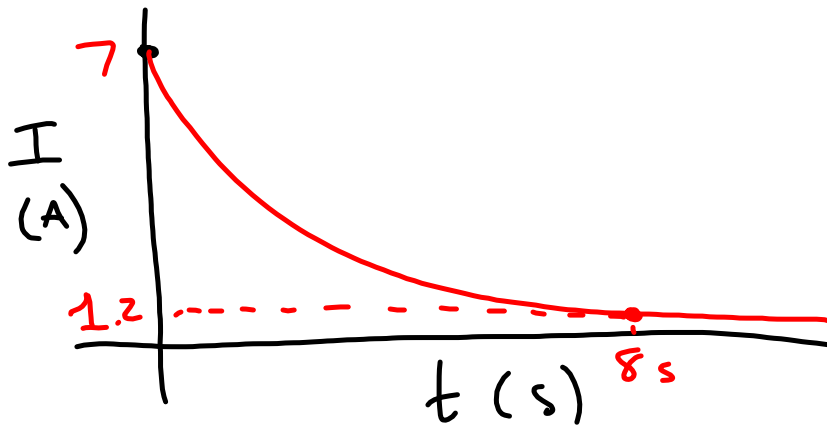
$$= 5021971124 \text{ m} \quad * \text{ oof.}$$



If C is
 $30\mu\text{F}$, find R

$$I = I_0 e^{-t/RC}$$

$$\ln\left(e^{-\frac{t}{RC}}\right) = \ln\left(\frac{I}{I_0}\right)$$

$$I_0 = 7\text{ A}$$


$$I = 1.2\text{ A}$$

$$t = 8\text{ s}$$

$$-\frac{t}{RC} = \ln\left(\frac{I}{I_0}\right)$$

$$R = \frac{-t}{\ln\left(\frac{I}{I_0}\right)C}$$

$$= 151206\Omega$$

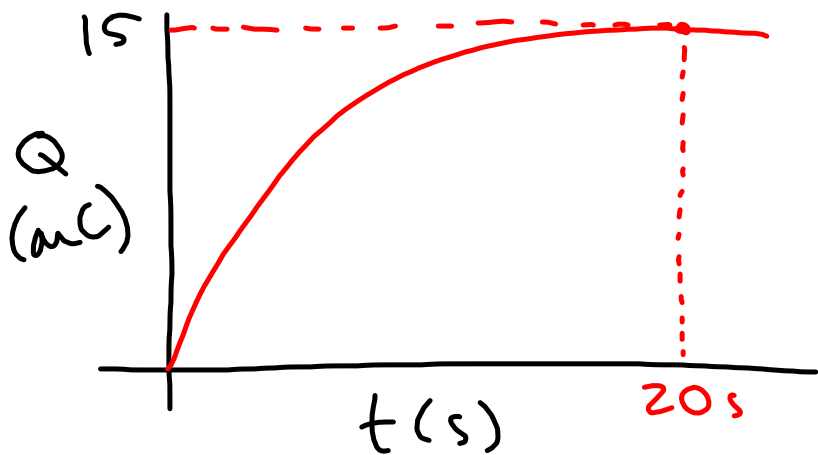

$$V = 10V$$

$$C = 1F$$

$$R = ?$$

$$Q = CV \left(1 - e^{-t/RC}\right)$$

$$\frac{Q}{CV} = 1 - e^{-t/RC}$$

$$\ln\left(e^{-t/RC}\right) = \ln\left(1 - \frac{Q}{CV}\right)$$

$$-\frac{t}{RC} = \ln\left(1 - \frac{Q}{CV}\right)$$

$$R = -\frac{t}{C \left[\ln\left(1 - \frac{Q}{CV}\right)\right]}$$

$$= 1.33E7 \Omega$$