

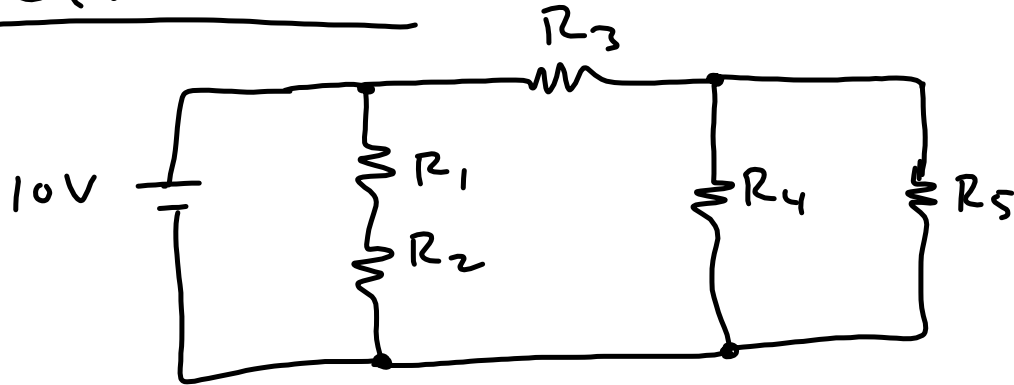
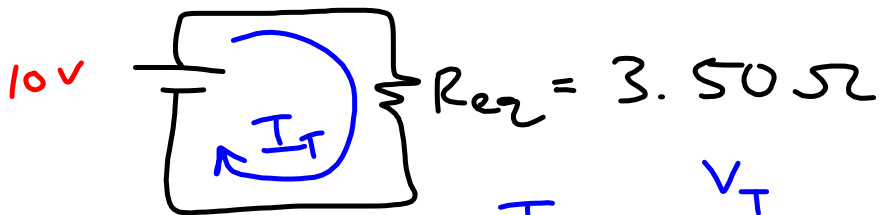


CIRCUITS

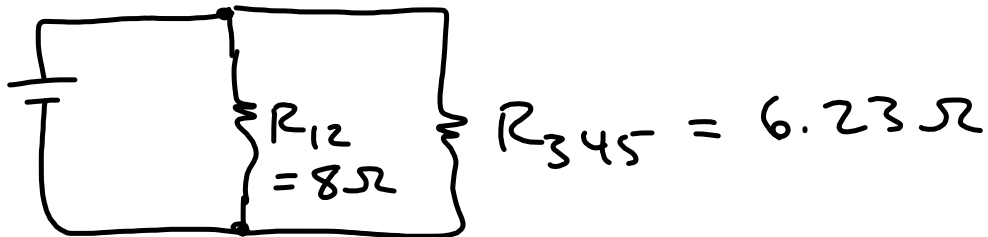


$$R_1 = 5\Omega \quad R_3 = 3\Omega \quad R_5 = 6\Omega$$

$$R_2 = 3\Omega \quad R_4 = 7\Omega$$

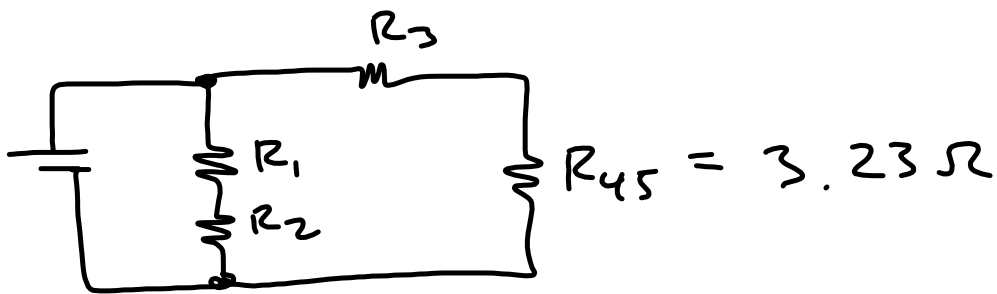


$$I_T = \frac{V_T}{R_{eq}} = 2.85A$$

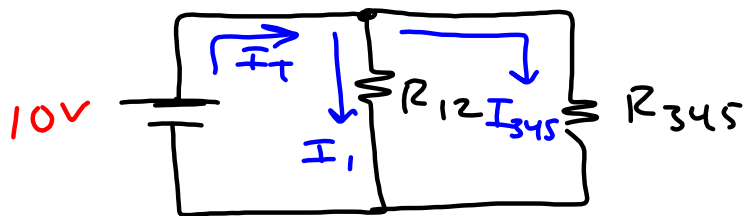

$$I_1 = \frac{V_T}{R_{12}} = 1.25 \text{ A}$$

$$I_{345} = 1.6 \text{ A}$$

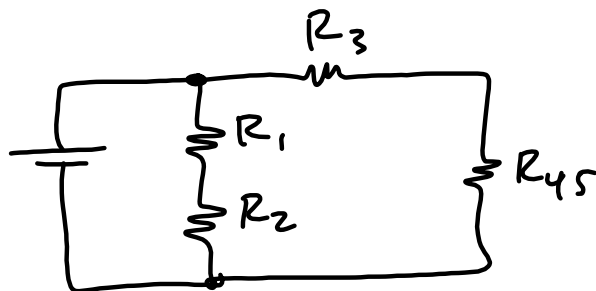


$$V_1 = I_1 R_1 = 6.25 \text{ V}$$

$$V_2 = 3.75 \text{ V}$$

$$V_3 = I_2 R_3 = 4.8 \text{ V}$$

$$V_{45} = I_2 R_{45} = 5.2 \text{ V}$$

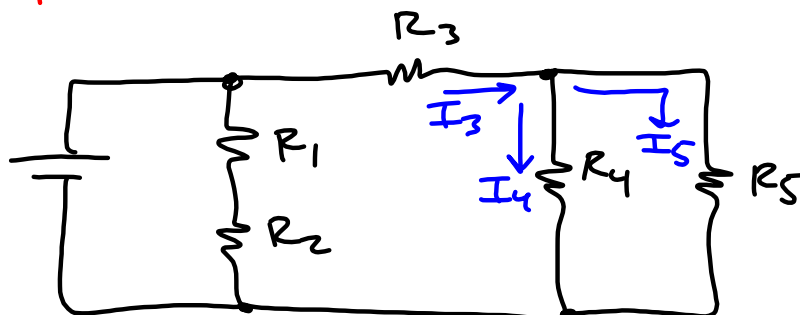

$$I_4 = \frac{V_{45}}{R_4} = 0.74 \text{ A}$$


$$I_5 = 0.86 \text{ A}$$

$$P_3 = I_3 V_3 = (1.6 \text{ A})(4.8 \text{ V}) = 7.68 \text{ W}$$

Energy Conservation:

(LOOP RULE) [Kirchhoff's Loop Rule]
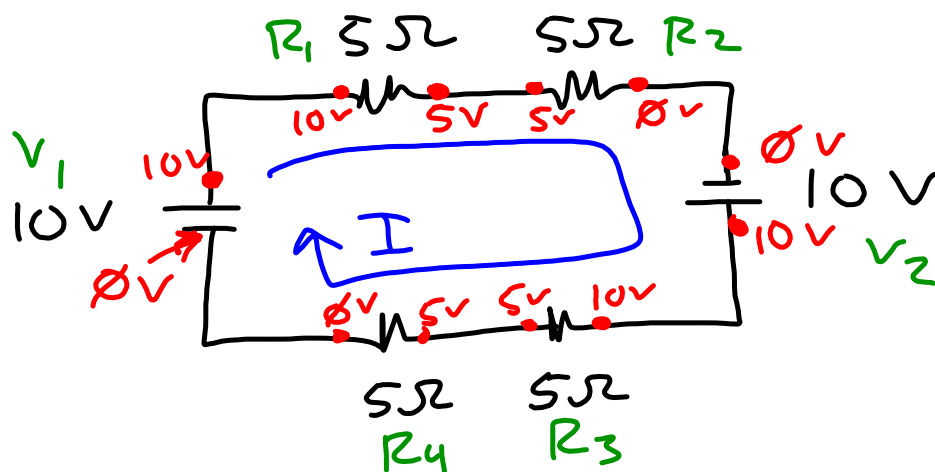
$$\Delta V_1 + \Delta V_2 + \dots = \emptyset$$



$$V_1 - IR_1 - IR_2 + V_2 - IR_3 - IR_4 = \emptyset$$

$$I = \frac{V_1 + V_2}{R_1 + R_2 + R_3 + R_4}$$

- $\mathcal{E} = \text{emf} = \text{electromotive force}$
 - * this is a bad name.
 - emf is actually energy per unit charge.
 - There is internal resistance of a battery.
-

KIRCHHOFF'S RULES:


1. Current Node Rule

Current into node = current out of node

2. Loop Rule

For a round-trip path,

$$\Delta V_1 + \Delta V_2 + \dots = 0$$

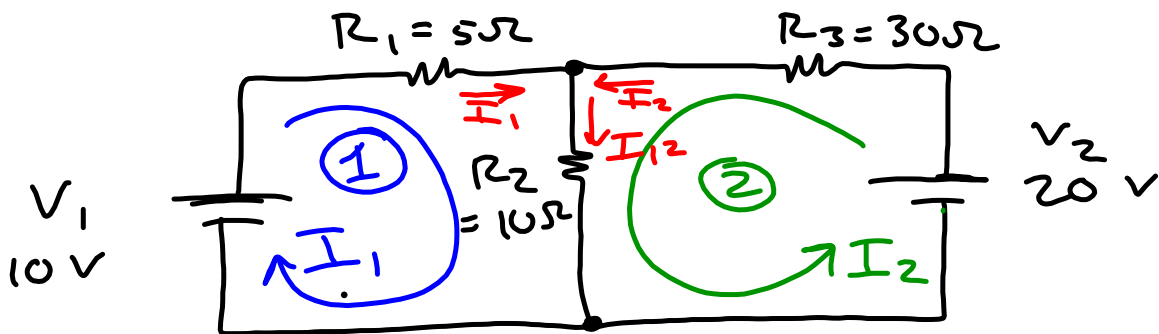

Loop

$$\textcircled{1} +V_1 - I_1 R_1 - I_{12} R_2 = 0$$

$$\textcircled{2} +V_2 - I_2 R_3 - I_{12} R_2 = 0$$


$$I_1 + I_2 = I_{12}$$

$$\frac{V_1}{R_1 + R_2} + \frac{V_2}{R_3 + R_2} = I_{12}$$

$$I_1 = \frac{V_1}{R_1 + R_2}$$

$$I_2 = \frac{V_2}{R_3 + R_2}$$

$$I_{12} = 1.167 \text{ A}$$

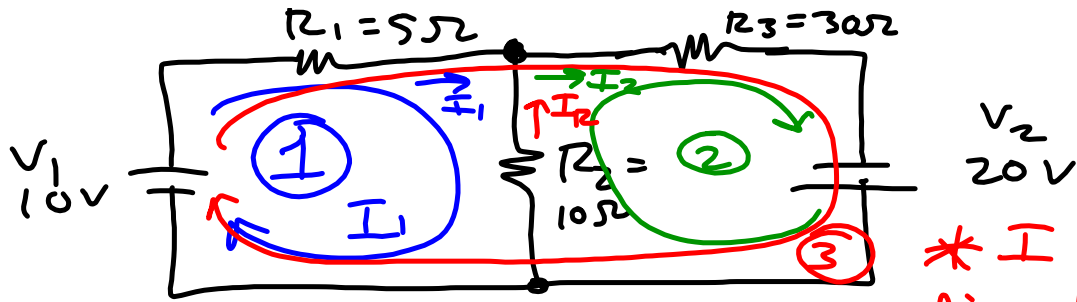

Find the current in R_2 .

$$\textcircled{1} +V_1 - I_1 R_1 - I_1 R_2 = \emptyset$$

$$\textcircled{2} +V_2 - I_2 R_3 - I_2 R_2 = \emptyset$$

* I chose direction of $I_{12} \rightarrow$ if I get a negative answer, I

chose wrong.

$$I_1 + I_{12} = I_2$$

$$I_1 = \frac{V_1}{R_1 + R_2} \quad I_2 = \frac{V_2}{R_3 + R_2}$$

$$I_{12} = I_2 - I_1$$

$$= \frac{V_2}{R_3 + R_2} - \frac{V_1}{R_1 + R_2}$$

$$= -0.17 \text{ A} \rightarrow \text{this is actually in the other direction!}$$