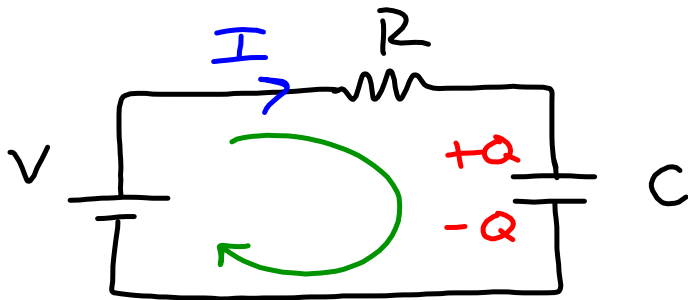


RC CIRCUIT DERIVATION



$$(\text{Battery}) - (\text{Resistor}) - (\text{Capacitor}) = \emptyset$$

$$V_B - V_R - V_C = \emptyset$$

$$+V - IR - \frac{Q}{C} = \emptyset$$

Final State of charged capacitor

$$Q = VC$$

Initial State:

$$I = \frac{1}{R} \left(V - \frac{Q}{C} \right)$$

$$\frac{dQ}{dt} = \frac{1}{R} \left(V - \frac{Q}{C} \right)$$

$$\frac{dQ}{dt} = \frac{V}{R} - \frac{1}{RC} Q$$

$$\frac{dQ}{dt} = \boxed{\frac{V}{R}}^{\text{constant}} - \frac{1}{RC} Q$$

$$I = I_0 e^{-at} \xrightarrow{\text{time}} \quad a = \text{constant}$$

↳ initial current

↳ current at some later time

$$\frac{d}{dt} \left[I = \frac{dQ}{dt} = \frac{V}{R} - \frac{1}{RC} Q \right]$$

$$\frac{dI}{dt} = -\frac{1}{RC} \frac{dQ}{dt}$$

$$\frac{dQ}{dt} = I$$

$$\frac{dI}{dt} = -\frac{1}{RC} I$$

$$\frac{dI}{dt} = -\frac{1}{RC} (I_0 e^{-at})$$

$$\frac{d}{dt} (I_0 e^{-at}) = -\frac{1}{RC} (I_0 e^{-at})$$

$$+ a(I_0 e^{-at}) = +\frac{1}{RC} (I_0 e^{-at})$$

$$a = \frac{1}{RC}$$

$$I = I_0 e^{-t/RC}$$