

## CIRCUITS; RESISTORS, CAPACITORS

- What do you know about these?
  - Use symbols, equations, words
- How do you connect a light, wire, and bulb to make the bulb light?
- How can we create the switching in our room?