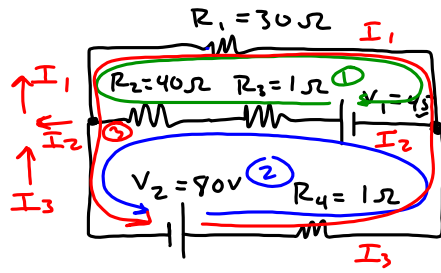


# KIRCHHOFF'S PRACTICE



Calculate the current in each branch.

$$\textcircled{1} \quad +V_1 - I_2 R_3 - I_2 R_2 - I_1 R_1 = \emptyset$$

$$\textcircled{2} \quad +V_2 - I_3 R_4 + V_1 - I_2 R_3 - I_2 R_2 = \emptyset$$

$$\textcircled{3} \quad +V_2 - I_3 R_4 - I_1 R_1 = \emptyset$$

$$I_2 + I_3 = I_1$$

\* We are basically done with Physics at this point... now on to Mathland!

$$V_2 - I_3 R_4 - (I_2 + I_3) R_1 = \emptyset$$

$$V_2 - I_3 R_4 - I_2 R_1 - I_3 R_1 = \emptyset$$

$$I_2 = \frac{1}{R_1} (V_2 - I_3 R_4 - I_3 R_1)$$

$$V_2 - I_3 R_4 - I_2 (R_3 + R_2) + V_1 = \emptyset$$

$$V_2 - I_3 R_4 - \left[ \frac{1}{R_1} (V_2 - I_3 R_4 - I_3 R_1) \right] (R_3 + R_2) + V_1 = \emptyset$$

$$V_2 - I_3 R_4 - \left( \frac{V_2}{R_1} - \frac{I_3 R_4}{R_1} - \frac{I_3 R_1}{R_1} \right) (R_3 + R_2) + V_1 = \emptyset$$

$$V_2 - I_3 R_4 - \frac{V_2 (R_3 + R_2)}{R_1} + \frac{I_3 R_4 (R_3 + R_2)}{R_1} + I_3 (R_3 + R_2) + V_1 = \emptyset$$

$$-I_3 R_4 + I_3 \frac{R_4 (R_3 + R_2)}{R_1} + I_3 (R_3 + R_2) = -V_1 - V_2 + \frac{V_2 (R_3 + R_2)}{R_1}$$

$$I_3 \left[ -R_4 + \frac{R_4 (R_3 + R_2)}{R_1} + (R_3 + R_2) \right] = -V_1 - V_2 + \frac{V_2 (R_3 + R_2)}{R_1}$$

$$I_3 = \frac{-V_1 - V_2 + \frac{V_2 (R_3 + R_2)}{R_1}}{-R_4 + \frac{R_4 (R_3 + R_2)}{R_1} + R_3 + R_2}$$

$$= \frac{-45V - 80V + \frac{80V (1\Omega + 40\Omega)}{30\Omega}}{-1\Omega + \frac{1\Omega (1\Omega + 40\Omega)}{30\Omega} + 1\Omega + 40\Omega}$$

$$= \frac{-45V - 80V + 109.33V}{-1\Omega + 1.37\Omega + 1\Omega + 40\Omega}$$

$$= \frac{-15.67V}{41.37\Omega}$$

$$= -0.38A$$

\* Not quite 1.7A ...

# CAPACITORS

- Store energy as an electric field.
  - Doesn't happen instantaneously, but does happen very quickly.
  - We can use the timing aspect to control circuits.
- Equations:

$$Q = C |\Delta V|$$

↓
↓
↓

charge                  capacitance                  electric potential

$$C = \frac{k \epsilon_0 A}{d}$$

$C \rightarrow$  capacitance

$\epsilon_0 \rightarrow$  permittivity of free space (constant)

$k \rightarrow$  dielectric constant

$A \rightarrow$  area


$d \rightarrow$  distance between plates

- Energy stored in a capacitor:

$$U_c = \frac{1}{2} Q \Delta V$$


$$U_c = \frac{1}{2} C (\Delta V)^2$$

- Capacitor - Only Circuit

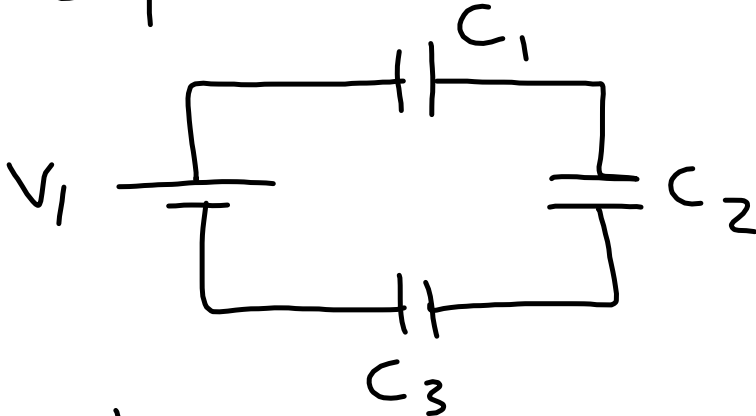

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_s} = \sum_i \frac{1}{C_i}$$

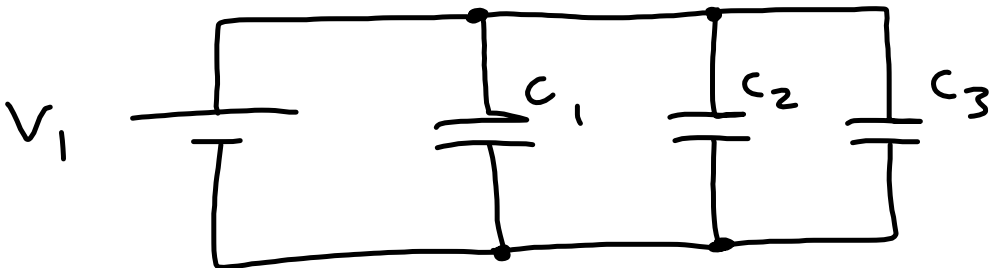

$$C_{eq} = C_1 + C_2 + C_3$$

$$C_p = \sum_i C_i$$