

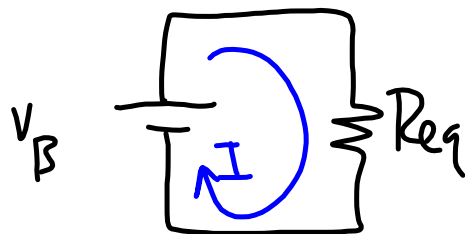


SERIES AND PARALLEL CIRCUITS

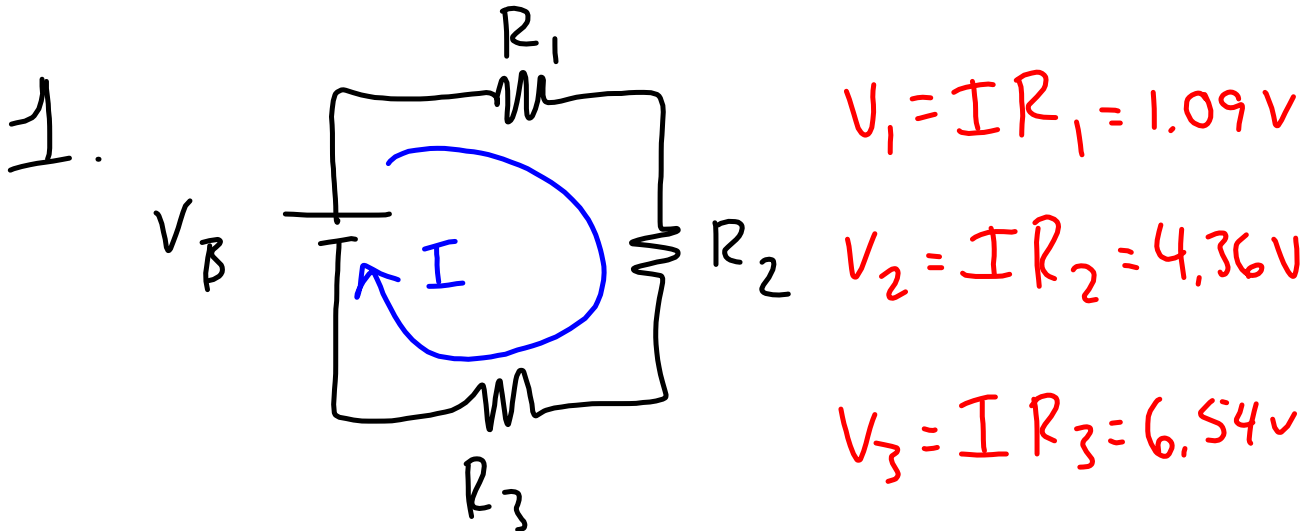

$$\begin{aligned}
 R_{eq} &= R_1 + R_2 + R_3 \\
 &= 1\Omega + 4\Omega + 6\Omega \\
 &= 11\Omega
 \end{aligned}$$
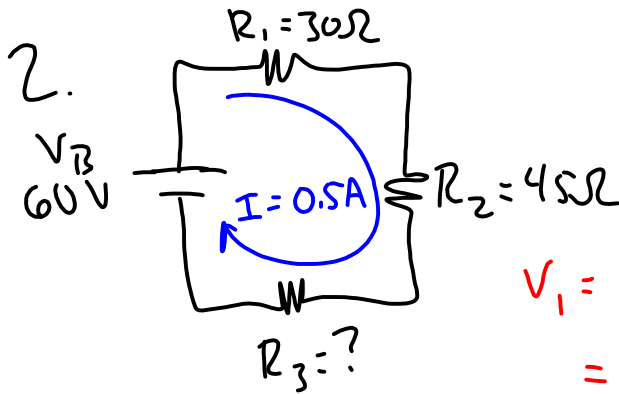
$$\underline{I} = \frac{V_B}{R_{eq}} = \frac{12 \text{ V}}{11\Omega} = 1.09 \text{ A}$$



$$V_1 = (0.5A)(30\Omega) = 15V$$

$$V_2 = (0.5A)(45\Omega) = 22.5V$$

$$V_B = V_1 + V_2 + V_3$$

$$V_3 = V_B - V_1 - V_2 = 60V - 15V - 22.5V = 22.5V$$

$$R_3 = \frac{V_3}{I} = \frac{22.5V}{0.5A} = 45\Omega$$

$$R_{eq} = R_1 + R_2 + R_3 = 30\Omega + 45\Omega + 45\Omega = 120\Omega$$

$$R_{eq} = \frac{V_B}{I} = \frac{60V}{0.5A} = 120\Omega$$




$$R_{eq} = R_1 + R_2 + R_3$$

$$R_3 = R_{eq} - R_1 - R_2 = 120\Omega - 30\Omega - 45\Omega = 45\Omega$$



Terms that are equivalent:

- Electric potential
- Potential difference
- Voltage
- Voltage drop


- Combination Circuits

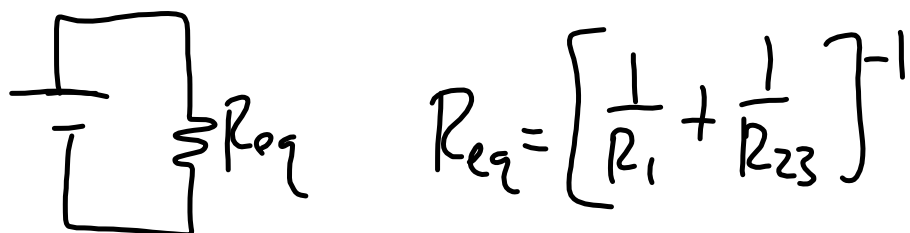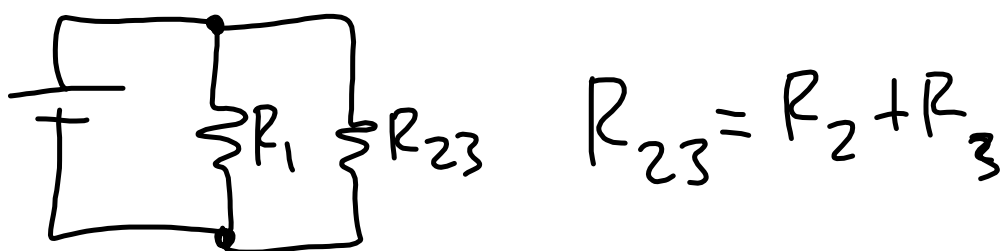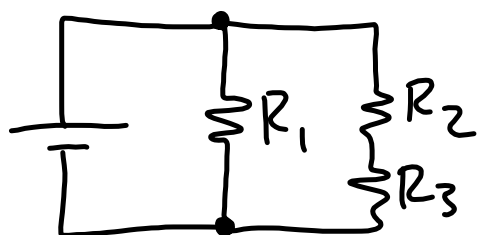

- Another combination circuit

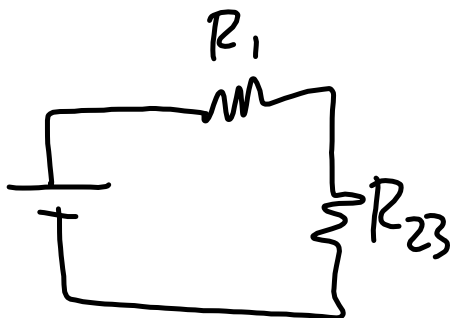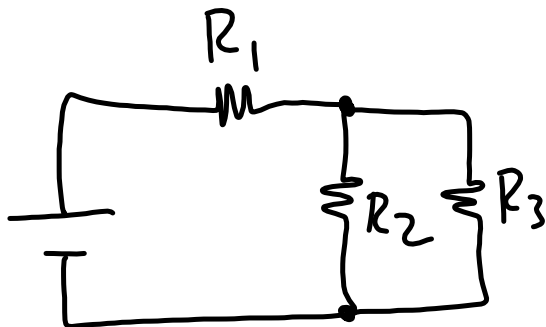
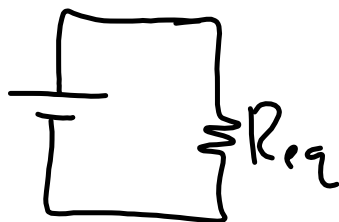
$$R_{23} = \left[\frac{1}{R_2} + \frac{1}{R_3} \right]^{-1}$$



$$R_{eq} = R_1 + R_{23}$$