

Batteries

- Have internal resistance \rightarrow usually $< 5\Omega$
- When internal resistance increases, battery cannot produce as much current.

Voltmeters

- Measure ACROSS a piece (this is in parallel)



Resistance is HIGH
(order of 1 million ohms)


We don't want current
in voltmeter, otherwise
we blow the fuse

Ammeter




Resistance is LOW
(less than 10Ω)


Charging/Discharging

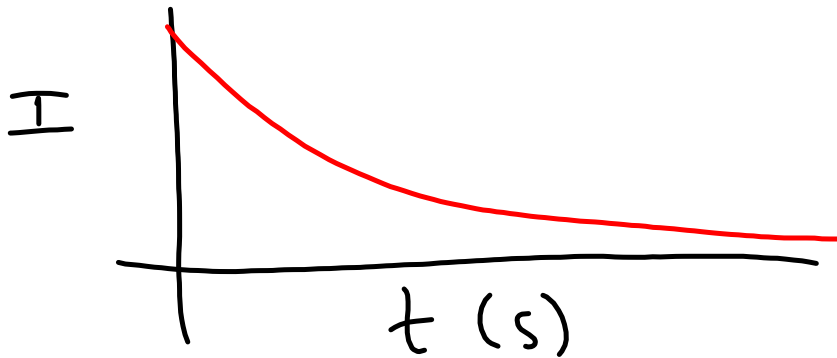

Charging

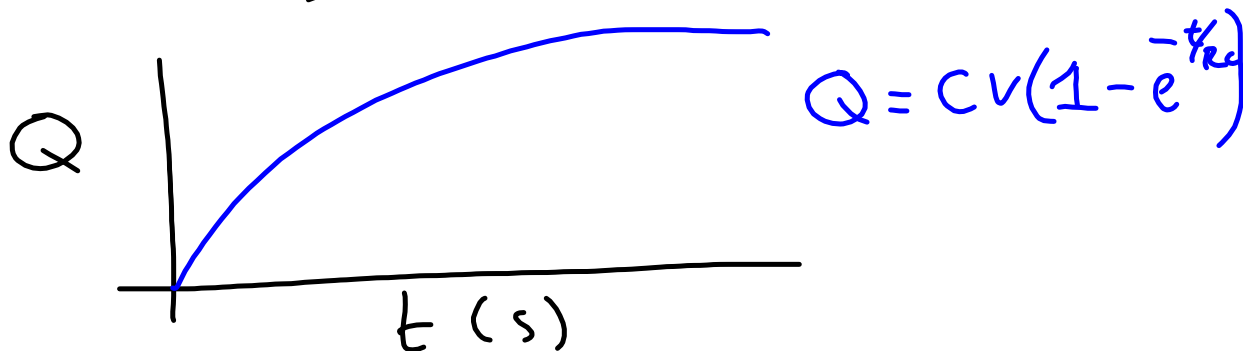

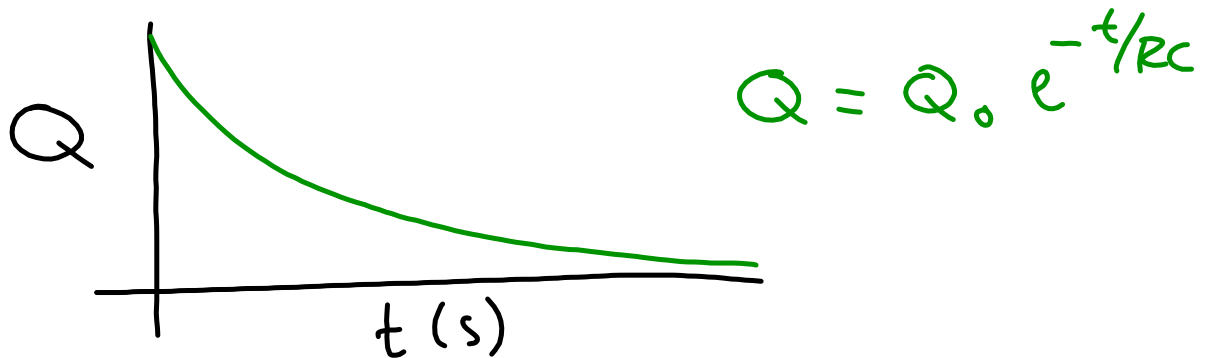Discharging \rightarrow RC only (no battery)



$$Q = q_1 + q_2 + \dots$$

(for "closed" circuit)