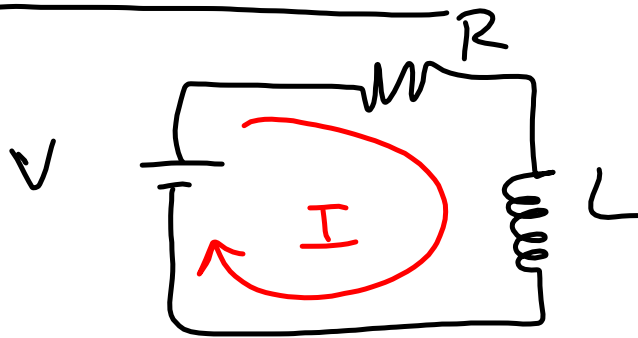


RL CIRCUITS




CHARGING

$$+V - IR - L \frac{dI}{dt} = 0$$


inductance

$$I = \frac{V}{R} \left[1 - e^{-(R/L)t} \right]$$
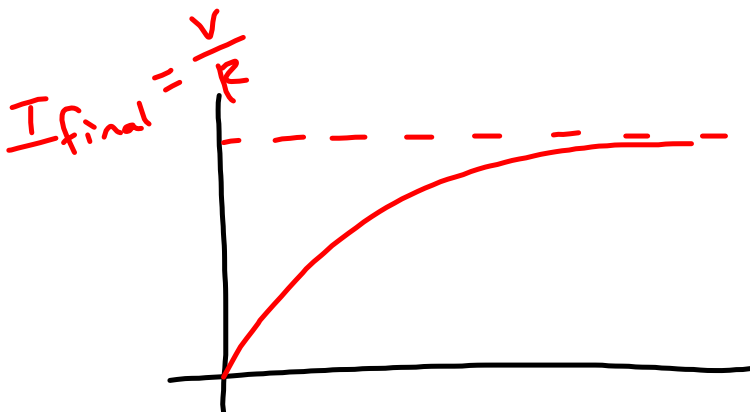
$$= I_{\text{final}} \left[1 - e^{-(R/L)t} \right]$$



DISCHARGING

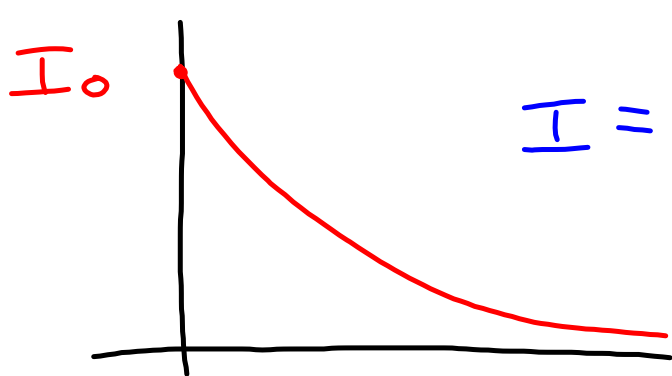

$$I = I_0 e^{-(R/L)t}$$

KNIGHT → ch. 30

Ex. 30.16

35

49