

CIRCUITS → What we know

- Ohm's Law
- Connect in parallel and series
- Battery
- Notation for drawing circuits
- Electrons flow from - to +
- Usually ignore resistance of wires
- Current in ^{parallel} branches is same for same valued resistors; voltage is same for series circuit